



REMARKS:

- Answers to problems must be returned separately. If you do not answer a problem, you must return at least a blank sheet for the problem.
- Please make sure your NAME and GROUP appears in every sheet you return.
- Calculators are not permitted.
- Time: 1h40'

Problem 1.1 (0.85 p.)

For the following logic function

$$f(a, b, c, d) = \sum_4 (1, 5, 6, 7, 9, 11, 13, 15)$$

- Find the most simplified logic expression as a **sum of products**
- Find the most simplified logic expression as a **product of sums**
- Implement the logic function with only 2-input NAND gates
- Implement f with a MUX4 (multiplexer with 4 data inputs) and additional logic gates

Problem 1.2 (0.3 p.)

Let $A = 10001011_2$ and $B = 19_{10}$.

- If A is a number in two's complement, which is the integer value of A?
- Represent B in two's complement. How many bits are needed?
- Perform the operations $A+B$ and $A-B$ in two's complement using 8 bits. Point out if there is overflow in any of these operations and why.


Problem 1.3 (0.85 p.)

Design an up/down module-6 counter. The counter will go from 0 to 5 or from 5 to 0. The counter has an input A that is used to select the counting direction, up ($A = 0$) or down ($A = 1$). The counting direction can be changed at any time.


The counter shall have a Cout output that activates in state 5 when counting up and in state 0 when counting down.

- Draw the State Transition Graph of the circuit.
- The circuit shall be implemented using T flip-flops. Find simplified expressions for the implementation of the circuit.
- Draw a circuit diagram.

1.1

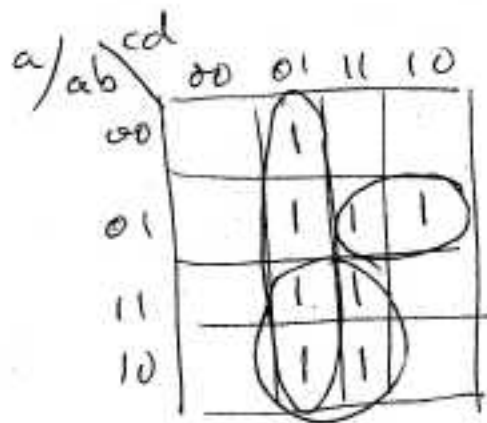


$$f = \bar{a}bc + ad + \bar{c}d$$

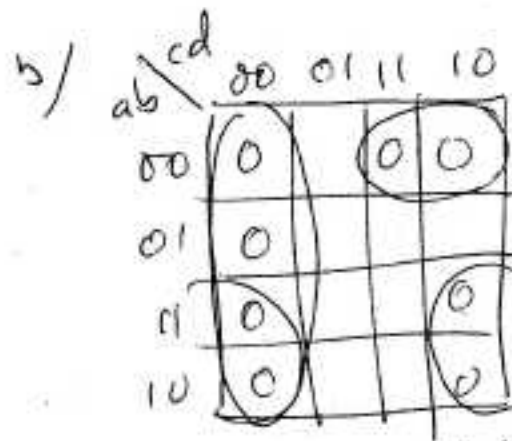


$$f = (a+b+\bar{c})(\bar{a}+d)(c+d)$$

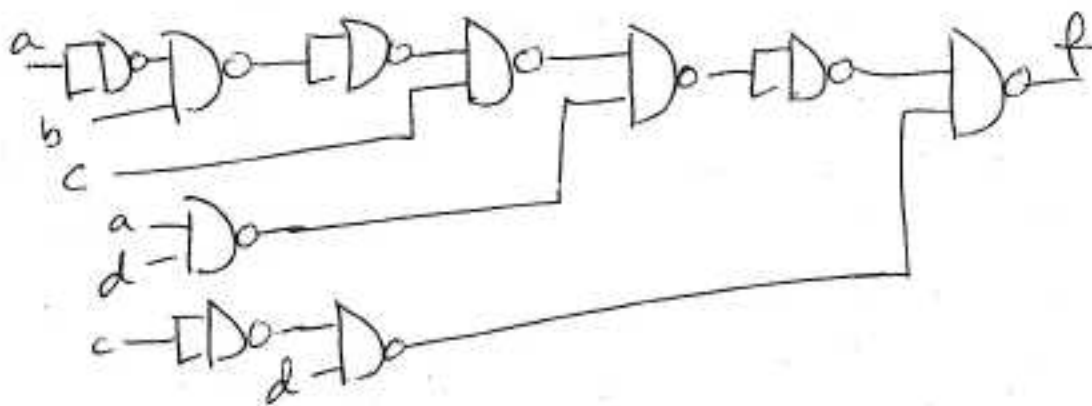c/ $f = \overline{\bar{a}bc + ad + \bar{c}d} = \overline{\bar{a}bc} \overline{ad} \overline{\bar{c}d}$



d/

abcd	f	
0000	0	
0001	1	$\bar{c}d$
0010	0	
0011	0	
0100	0	
0101	1	$c+d$
0110	1	
0111	1	
1000	0	
1001	1	d
1010	0	
1011	1	
1100	0	
1101	1	d
1110	0	
1111	1	

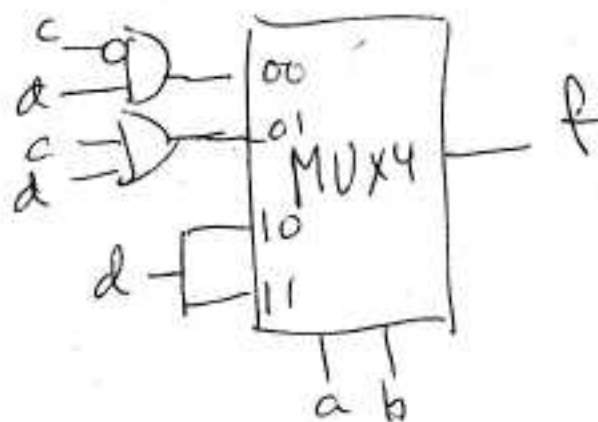

1.2

a) $A = 10001011_2 = -117_{10}$

b) $B = 19_{10} = 00010011_2$ (needs at least 6 bits = 010011)

c)



$$\begin{array}{r} A = 10001011 \\ + B = 00010011 \\ \hline 10011110 = -18 \end{array}$$

$$\begin{array}{r} A = 10001011 \\ + \bar{B} = 11101101 \\ \hline \times 01111000 = 120 \end{array}$$

There is overflow because the signs of the operands do not coincide with the sign of the result

wrong

1.3

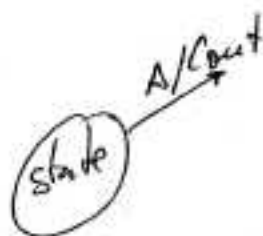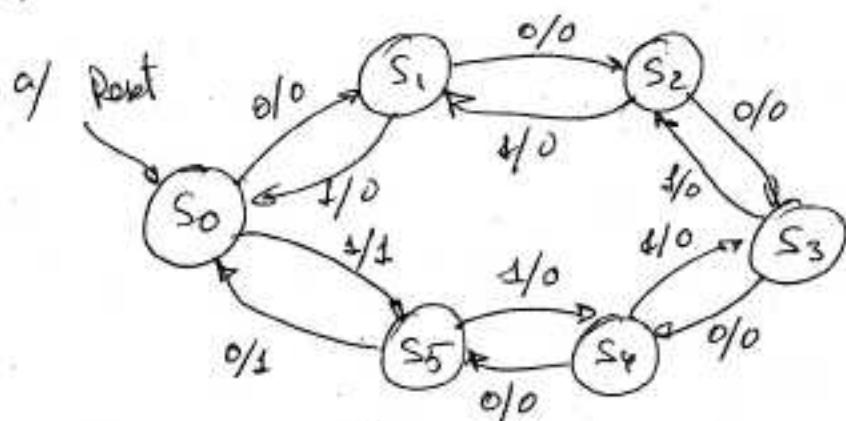

b/

A	q_2	q_1	q_0	q_2^+	q_1^+	q_0^+	T_2	T_1	T_0	Count
0	0	0	0	0	0	1	0	0	1	0
0	0	0	1	0	1	0	0	1	1	0
0	0	1	0	0	1	1	0	0	1	0
0	0	1	1	1	0	0	1	1	1	0
0	1	0	0	1	0	1	0	0	1	0
0	1	0	1	0	0	0	1	0	1	1
0	1	1	0	x	x	x	x	x	x	x
0	1	1	1	x	x	x	x	x	x	x
1	0	0	0	1	0	1	1	0	1	1
1	0	0	1	0	0	0	0	0	1	0
1	0	1	0	0	0	1	0	1	1	0
1	0	1	1	0	1	0	0	0	1	0
1	1	0	0	0	1	1	1	1	1	0
1	1	0	1	1	0	0	0	0	1	0
1	1	1	0	x	x	x	x	x	x	x
1	1	1	1	x	x	x	x	x	x	x

A, q_2

q_1, q_0	00	01	11	10
00			1	
01		1	x	x
11	1		x	x
10	1			

A, q_1

q_2, q_0	00	01	11	10
00	1	1		
01		x	x	
11	1	x	x	
10				1

A, q_0

q_2, q_1	00	01	11	10
00	1	1	1	1
01	1	1	x	x
11	1	1	x	x
10	1	1	1	1

$$T_2 = q_1 q_0 \bar{A} + \bar{A} q_2 q_0 + A \bar{q}_1 \bar{q}_0$$

$$T_1 = \bar{A} \bar{q}_2 q_0 + A q_2 \bar{q}_0 + A q_1 \bar{q}_0$$

$$T_0 = 1$$

$A \backslash \begin{matrix} q_1 q_0 \\ 00 & 01 & 11 & 10 \end{matrix}$				
00				
01		1	X	X
11			X	X
10	1			

$$Count = A \bar{q}_2 \bar{q}_1 \bar{q}_0 + \bar{A} q_2 q_0$$

c/

