

PROBLEM 1

Complete the enclosed schedule, from the circuit of the figure 1.


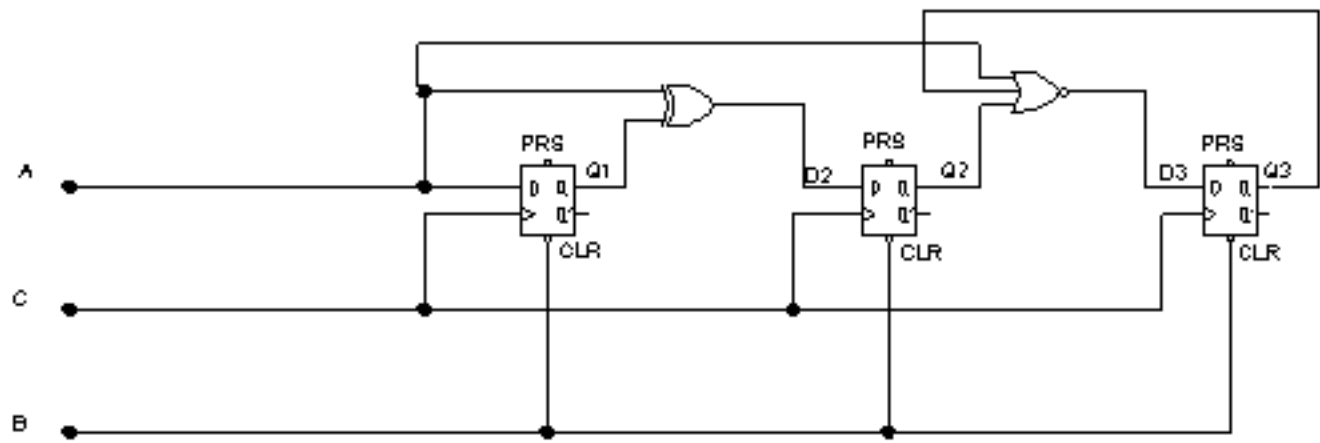


Figure 1

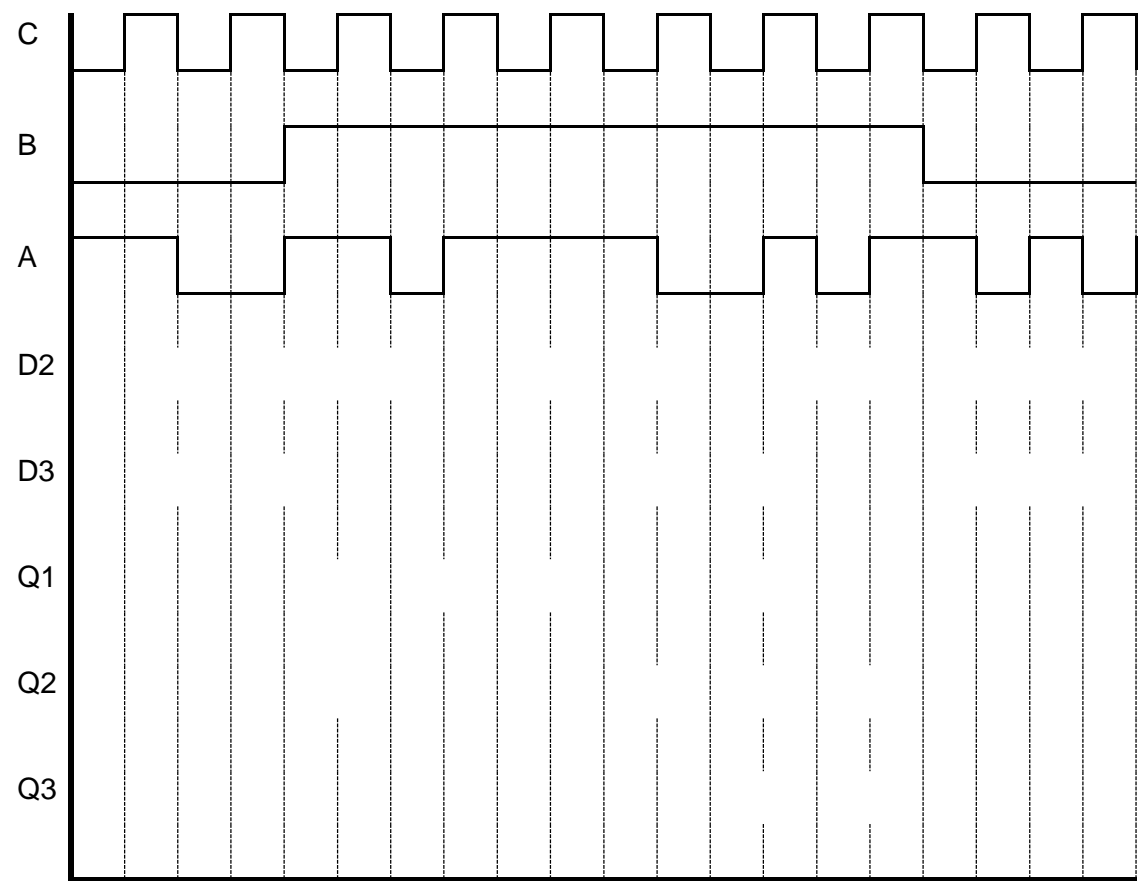

PROBLEM 2

Consider the circuit of the **Figure 2.1** Where Clear and A are the input signals and S is the output signal. B, Q₀ and Q₁ Are the signs at the points indicated.

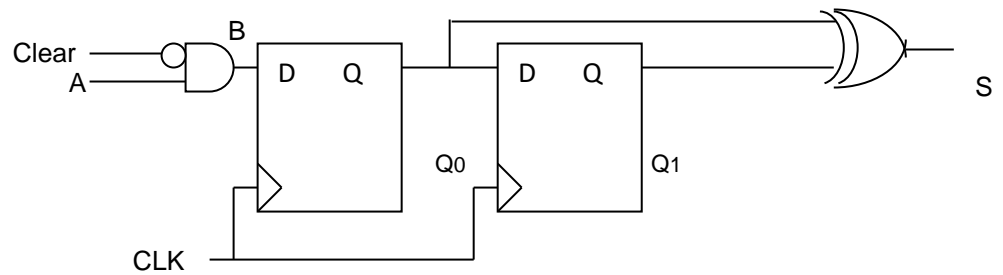


Figura 2.1

Complete the schedule of the **Figure 2.2**, knowing that the initial state of the flip-flop is 0.

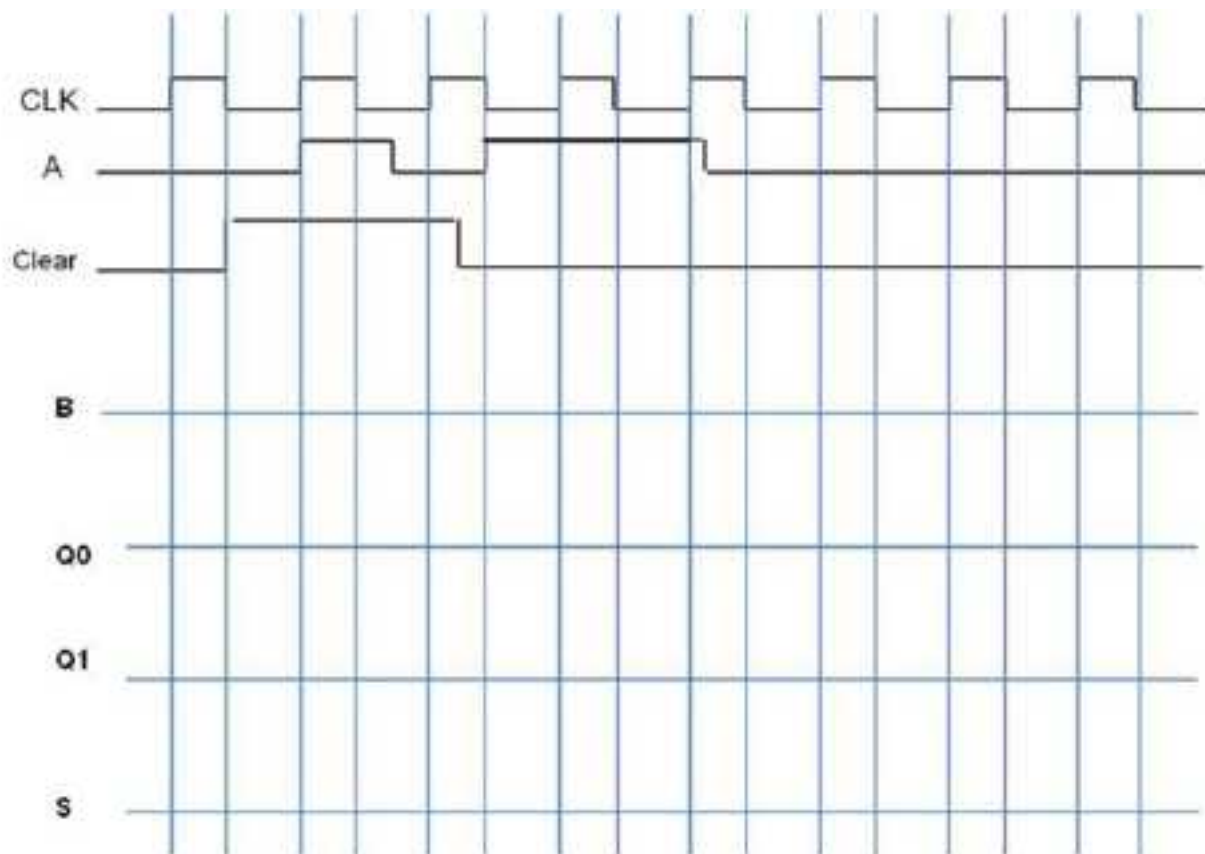


Figure 2.2

PROBLEM 3


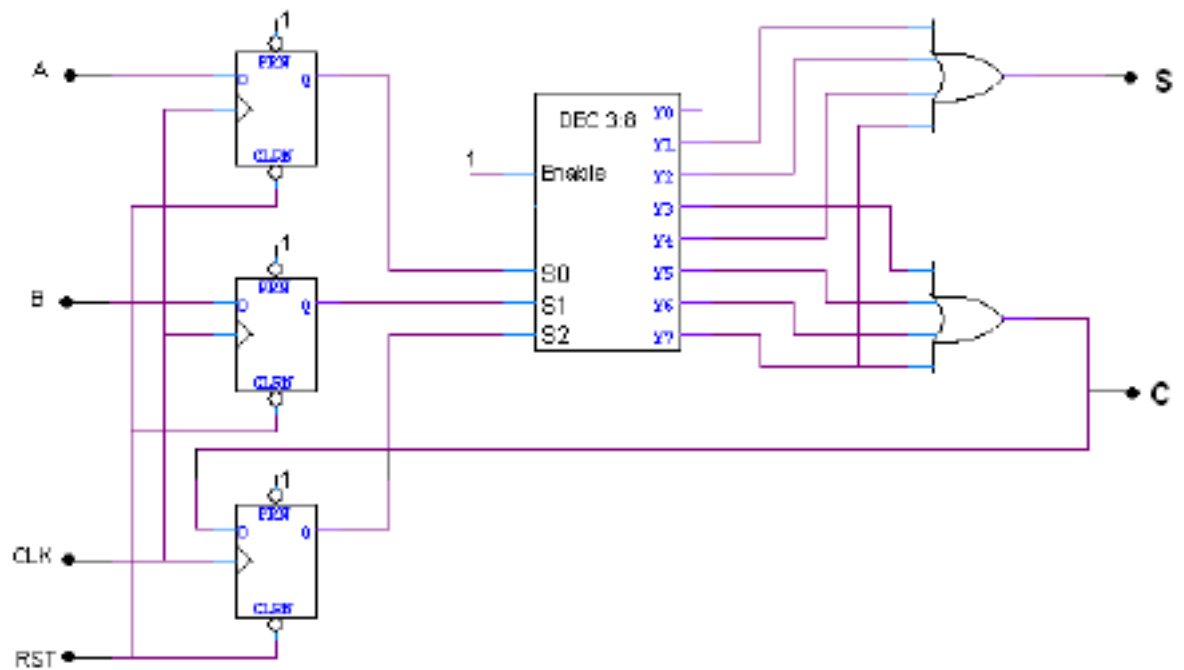


Figure 3


Taking the circuit of the figure 3:

- Get the simplified $S(S2, S1, S0)$ function.
- Get the simplified function $C(S2, S1, S0)$ in the form of a sum of products.
- Complete the following schedule. Use the necessary additional lines.

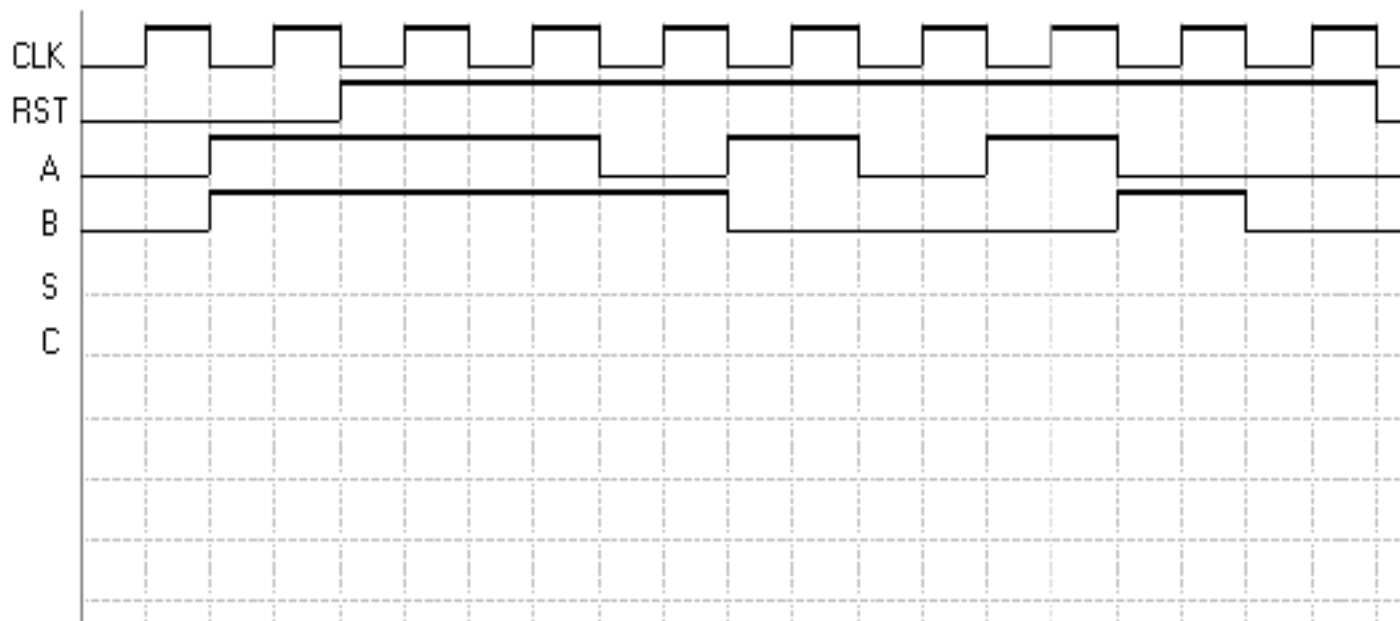


PROBLEM 4

For the following circuit:

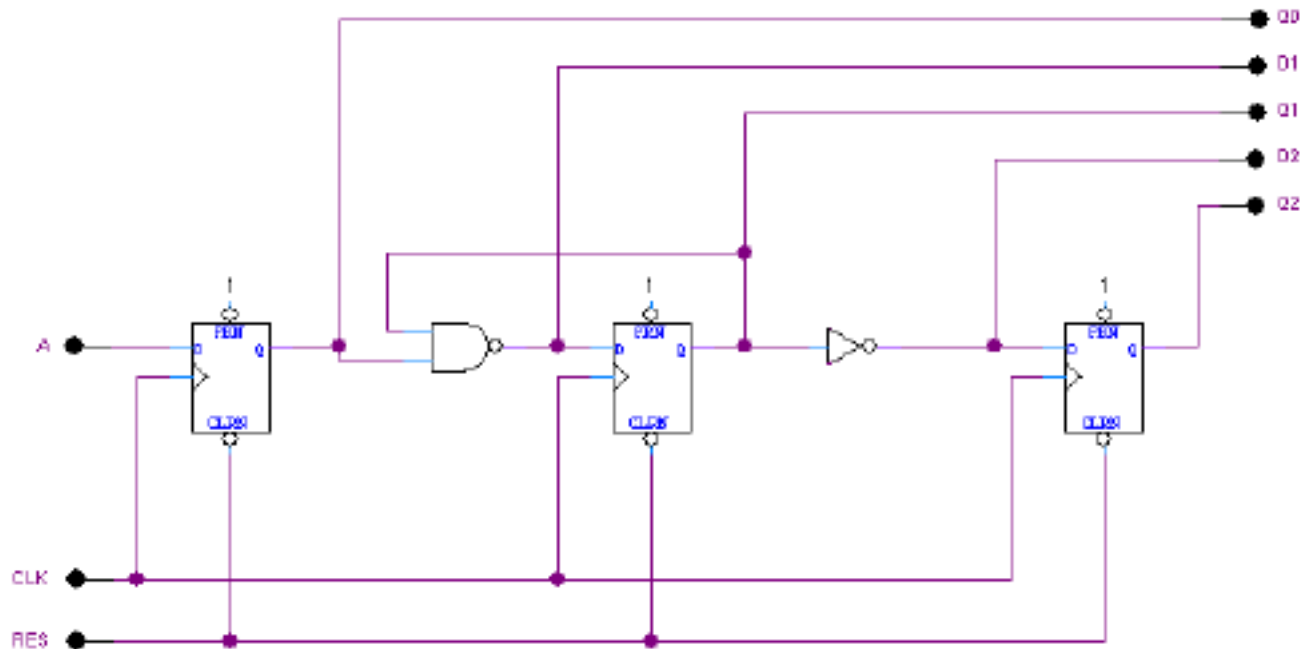

Complete the following timeline:

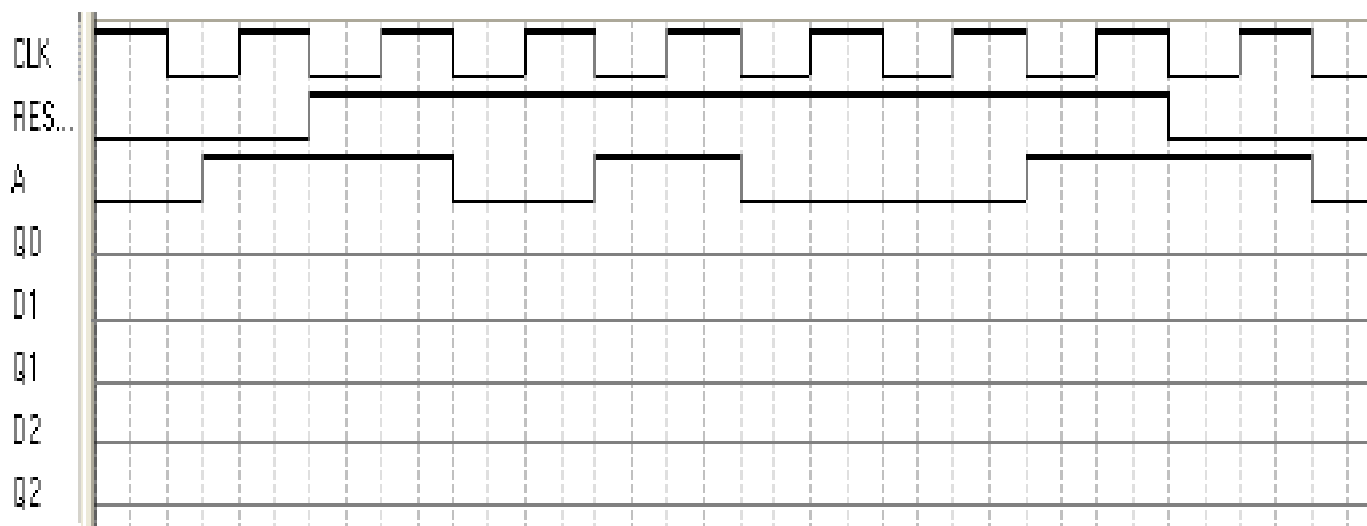

PROBLEM 5

In the circuit of the figure 5 It shows a sequential system based on bistables and logic doors.

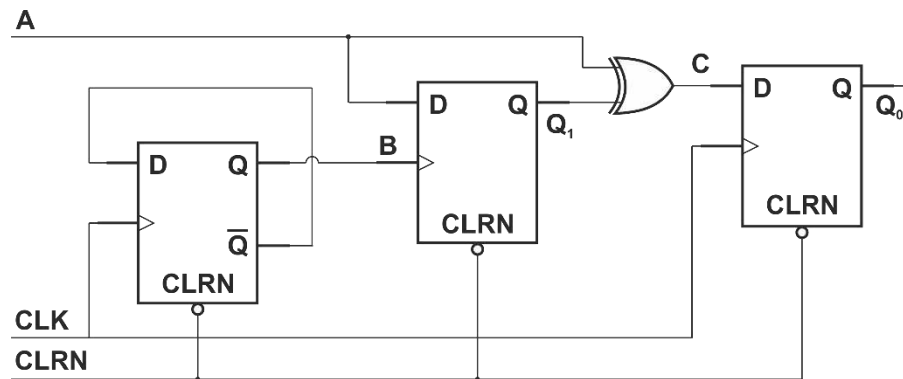


Figura 5

- Describe the table of truth for the bistable D of the circuit of the **Figure 5.1**. Use as input signals: CLRN, CLK and D, and as outputs Q_{t+1} and \bar{Q}_{t+1} .
- complete the enclosed schedule corresponding to the circuit of the **Figure 5.2** and indicate what **Operation** He's doing the same. Suppose the initial state is $Q = 0$.

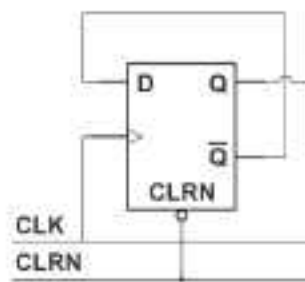


Figure 5.1

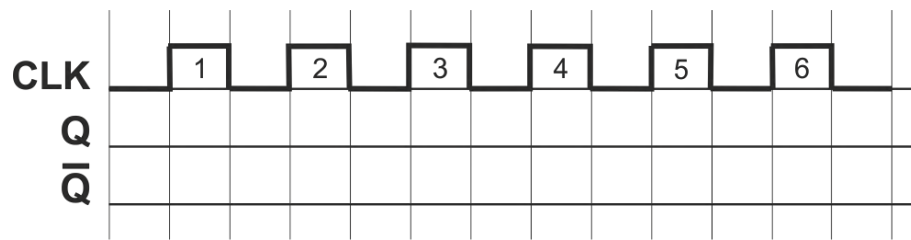


Figure 5.2. Timeline for the circuit

- From the results of the preceding paragraphs, complete the enclosed timetable for the operation of the circuit of the **Figure 5**.

