



IMPORTANT:

Each problem or question must be solved in a different sheet of paper, do not answer two problems on the same sheet. Write your name and group in every sheet. Hand in a sheet for each problem/question, even if you did not answer it. Calculators are not allowed.

Time: 3h

Problem 1 (2.5 points)

The circuit shown in the Figure.1 corresponds to the arithmetic unit of a data path. This unit performs an operation on two numbers A and B having two bits each.

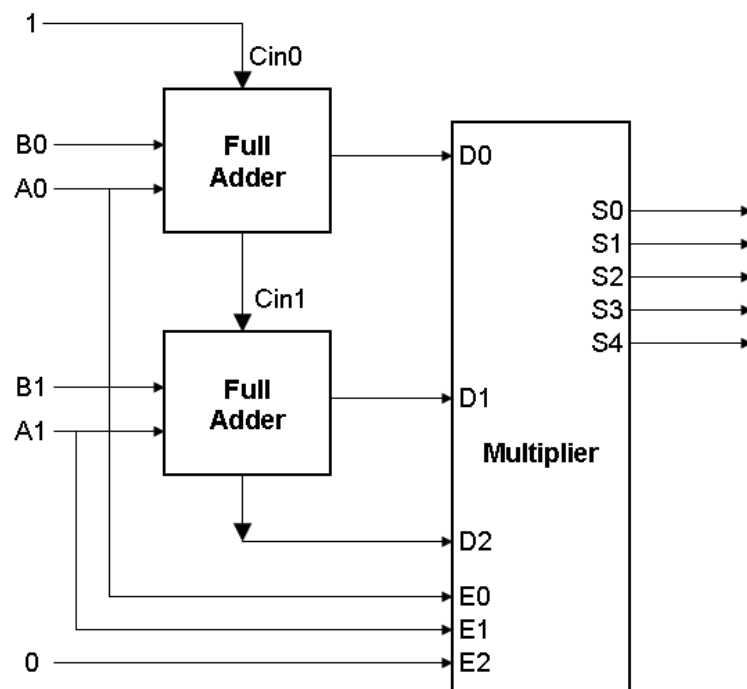


Figure.1

We want to resynthesize this control unit, taking into account that the data A never reaches 3.

- Identify the arithmetic operation performed by the unit.
- Provide in 'Decimal' the table for the possible input values of A and B along with the outputs D and S.
- Provide the 'Binary' truth table of the whole unit, taken as inputs the possible values of A and B and output S. Consider the restriction of data A.
- Synthesize the function S0 with the minimum number of NAND gates.
- Synthesize the function S1 with a 'Decoder' with low active outputs and minimum possible number of additional logic gates.
- Synthesize the function S2 with a 'Multiplexer' having 2-selection inputs and minimum possible number of additional logic gates.
- Synthesize the function S3 with the minimum possible number of NOR gates.




NAME: _____

GROUP: _____

Problem 2 (2,5 points)

For the circuit of the figure:

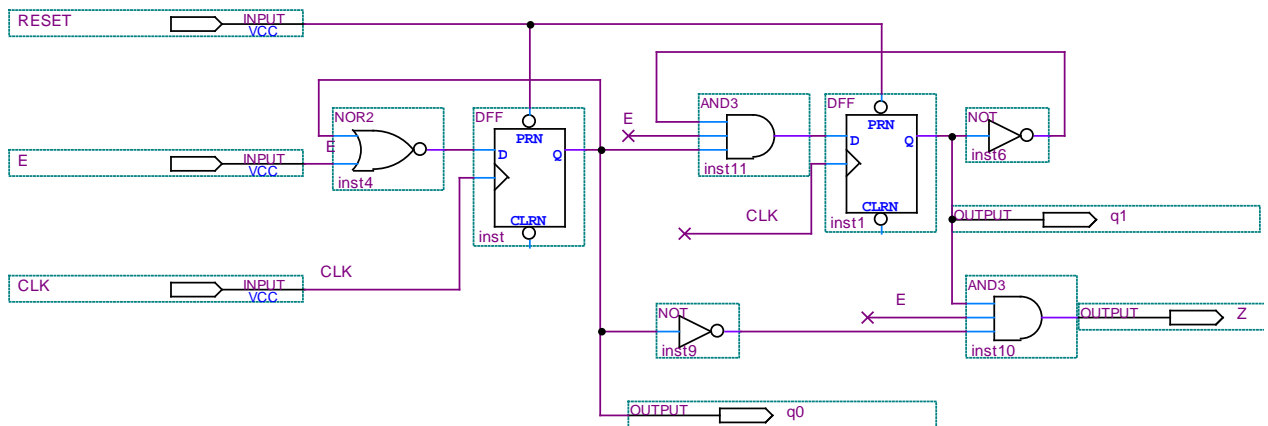


- Write the logic expressions of the inputs of the flip-flops and the outputs.
- Fill the following table and draw the state transition graph, considering the provided state encoding.

Q1	Q0	
0	0	E0
0	1	E1
1	0	E2
1	1	E3

Q1	Q0	E	D1	D0	Z	Q1 ⁺	Q0 ⁺

 - Fill the following chronogram, considering that the flip-flops are rising edge triggered:





Universidad Carlos III de Madrid

Degrees in Engineering: Telecommunication Technologies, Communication Systems,
Telematics, Audiovisual Systems
DIGITAL ELECTRONICS

Final exam – May 23th, 2013

NAME: _____

GROUP: _____

IMPORTANT:

Each problem or question must be solved in a different sheet of paper, do not answer two problems on the same sheet. Write your name and group in every sheet. Hand in a sheet for each problem/question, even if you did not answer it. Calculators are not allowed.

Problem 3 (2 points)

Answer to the following questions, circling the correct answer. If you make a mistake, correct it so that the answer is clear and not ambiguous, or it will be considered as not correct.

The score in this question will be proportional to:

$$\text{Number of correct answers} - (\text{Number of wrong answers})/3$$

(Not answered questions are not considered wrong)

1. Tri-state buffers allow:
 - a) Increasing the number of inputs that can be connected to an output.
 - b) Connecting several outputs without short circuits.
 - c) Storing a bit while the buffer is powered.
 - d) None of the above.
2. The noise margin is:
 - a) Intervals of voltages associated to the different logic levels.
 - b) The difference between the power supply voltage and the admissible input voltage in a logic gate.
 - c) The difference between the noise voltage in the output and the noise voltage in the input of a logic gate.
 - d) None of the above.
3. ASICs are:
 - a) Integrated circuits that can be programmed just once.
 - b) Re-programmable Integrated Circuits.
 - c) Application Specific Integrated Circuits.
 - d) None of the above.
4. The Status Register of a microprocessor contains:
 - a) The result of the last operation.
 - b) An operand of the operation to be performed.
 - c) Next instruction to execute.
 - d) None of the above.



Universidad Carlos III de Madrid

Degrees in Engineering: Telecommunication Technologies, Communication Systems,
Telematics, Audiovisual Systems
DIGITAL ELECTRONICS

Final exam – May 23th, 2013

5. The Program Counter of a Microprocessor contains:
 - a) The number of executed instructions.
 - b) The size of the program being executed.
 - c) The memory address of the next instruction to execute.
 - d) None of the above.

6. The Von Neumann Architecture is characterized by:
 - a) It can access program memory and data memory at the same time.
 - b) It uses the same address BUS to access data and program addresses.
 - c) It has an independent register bank for input/output operations.
 - d) None of the above.

7. If an ALU performs the AND operation with the operands 0x63 and 0x45 the result will be:
 - a) 0x12
 - b) 0x41
 - c) 0xA8.
 - d) None of the above.

NOTE: "0x" means HEXADECIMAL

8. The size of the instructions in a microprocessor:
 - a) It is the same for all of them.
 - b) It is the same as the size of the memory word.
 - c) It is a multiple of the size of the memory word.
 - d) None of the above.

9. To program in assembly language:
 - a) It is necessary to know the microprocessor architecture.
 - b) It is necessary to know the operation codes of the instructions.
 - c) It is necessary to know high level programming languages.
 - d) None of the above.

10. The controller circuit of a microprocessor:
 - a) is a combinational circuit.
 - b) is a synchronous sequential circuit.
 - c) is an asynchronous sequential circuit.
 - d) None of the above.



Universidad Carlos III de Madrid

Degrees in Engineering: Telecommunication Technologies, Communication Systems,
Telematics, Audiovisual Systems
DIGITAL ELECTRONICS

Final exam – May 23th, 2013

NAME: _____

GROUP: _____

Problem 4 (3 points)

A microprocessor system has a data memory of 256M x 16 bits. In this memory the lowest part is read-only and the highest part is RAM memory. There are 64M addresses of ROM and 192M addresses of RAM.

To implement this memory the following chips are available:

2 chips de ROM de 32M x 16 bits	IC1, IC2
2 chips de RAM de 64M x 8 bits	IC3, IC4
1 chip de RAM de 128M x 16 bits	IC5

- Draw the memory map of the system, indicating the first and last addresses of each module, both in binary and hexadecimal.
- Draw the circuit with all the modules and connections, using a 2:4 decoder with active-low outputs for the addresses decoding.

Note: All the control inputs of the memories are active-low.