
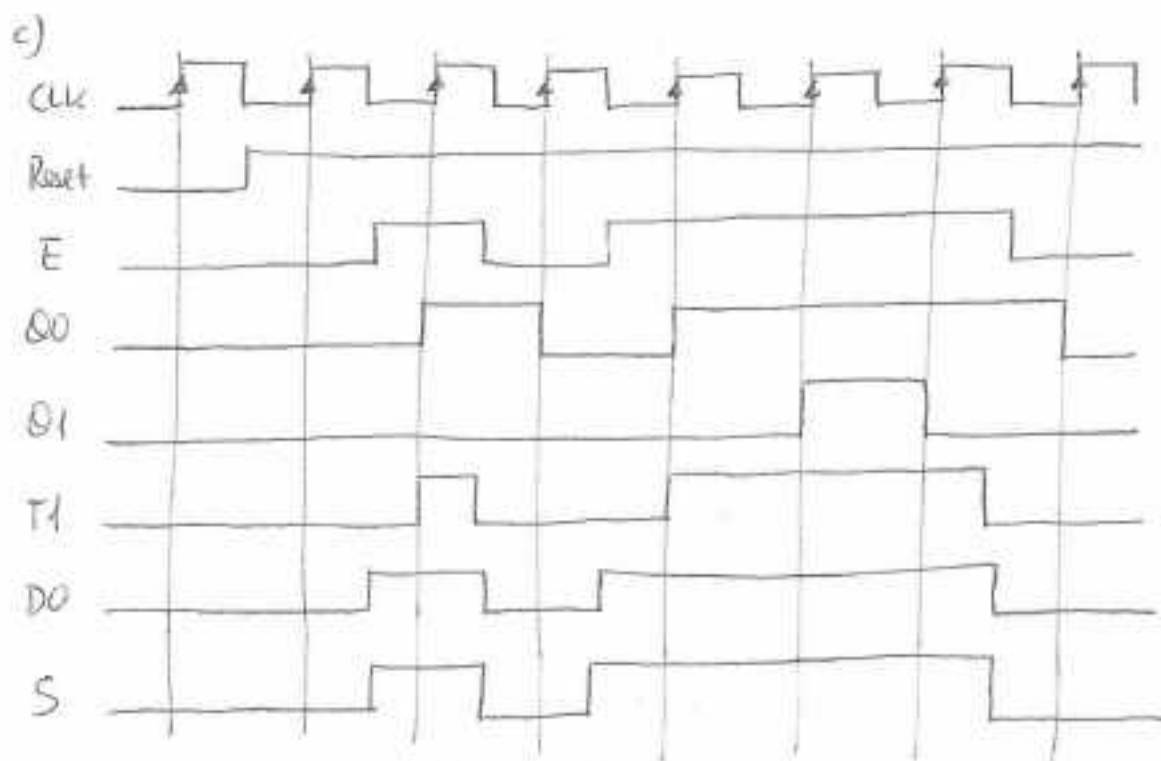


* Question 3

- a) It is a Mealy circuit because the output depends on the input and the state.
 b) Output function: $S = E + Q_1$
 State functions: $DQ = E$
 $T_1 = E \cdot Q_0$

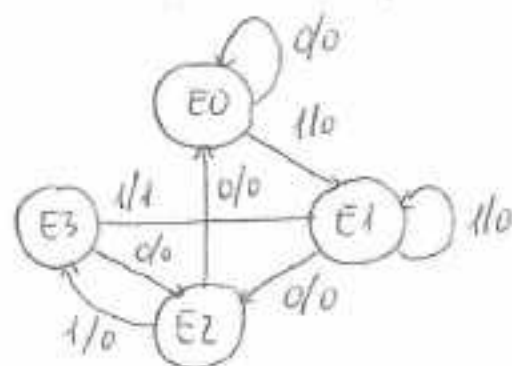

* Question 4



- a) There are 1 input and 1 output, for example, X for the input and Y for the output.
 b) There are 4 states (E_0, E_1, E_2, E_3) and the number of flip-flops must fulfill the next expression: $2^n \geq N$ | $N = \text{number of states}$ | $N = 4 \Rightarrow n = 2$: You need 2 flip-flops.
 $n = \text{number of flip-flops}$

For the state encoding, considering the requirement of the enumeration, the only solution is:

State	Q_0	Q_1	
E_0	0	0	= 0 in decimal
E_1	0	1	= 1 in decimal
E_2	1	0	= 2 in decimal
E_3	1	1	= 3 in decimal