



REMARKS:

- Answers to problems must be returned separately. If you do not answer a problem, you must return at least a blank sheet for the problem.
- Please make sure your NAME and GROUP appears in every sheet you return.
- Calculators are not permitted.
- Time: 1h40'

Problem 1.1 (0.85 p.)

For the following logic function

$$f(a,b,c,d) = (a+b)c\bar{d} + \bar{b}(a\bar{d} + \bar{c})$$

- Find the canonical forms of the function
- Find the most simplified logic expression as a **product of sums**
- Implement the logic function with only 2-input NOR gates
- Implement f with a decoder and additional logic gates.
- Implement f with a MUX4 (multiplexer with 4 data inputs) and additional logic gates

Problem 1.2 (0.3 p.)

Let $A = E3_{16}$ and $B = 96_{10}$.

- If A represents a number in sign-magnitude, which is the integer value of A?
- If A represents a number in two's complement, which is the integer value of A?
- Represent B in two's complement. How many bits are needed?
- Using two's complement representations for the numbers, perform the operations $A+B$ and $A-B$. Point out if there is overflow in any of these operations and why.

Problem 1.3 (0.85 p.)

Design a sequential circuit that has a single input X and a single output Z. The circuit must comply with the following requirements:

- Initially, $Z = 0$.
- The output will be activated ($Z = 1$) when $X = 1$ for at least 3 consecutive clock cycles. Once $Z = 1$, the output will remain activated until $X = 0$ for at least 3 consecutive clock cycles.


Example:

X:	0 0 0 1 1 0 1 1 1 0 1 0 0 1 1 0 0 0 0 0 1 1 1 1 1 0 0 0 0
Z:	0 0 0 0 0 0 0 0 1 1 1 1 1 1 1 1 0 0 0 0 0 1 1 1 1 1 0 0


- Draw the State Transition Graph of the circuit
- Consider an implementation using D flip-flops and encoding the states in natural binary. How many flip-flops are necessary?
- Write the transitions table
- Find simplified expressions for the implementation of the circuit
- Draw a circuit diagram

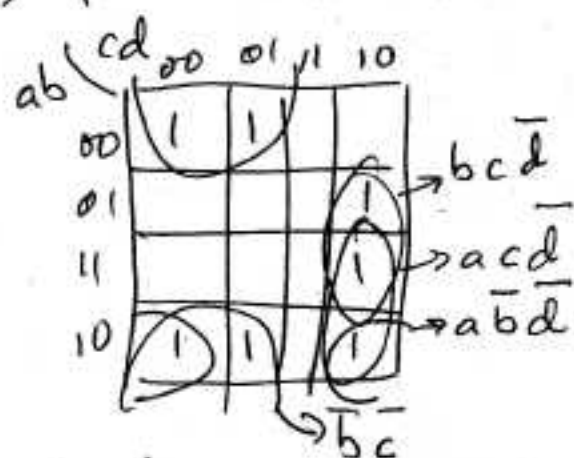1.1

$$a) f = (a+b) c \bar{d} + \bar{b} (a \bar{d} + \bar{c}) = a c \bar{d} + b c \bar{d} + a \bar{b} \bar{d} + \bar{b} \bar{c}$$




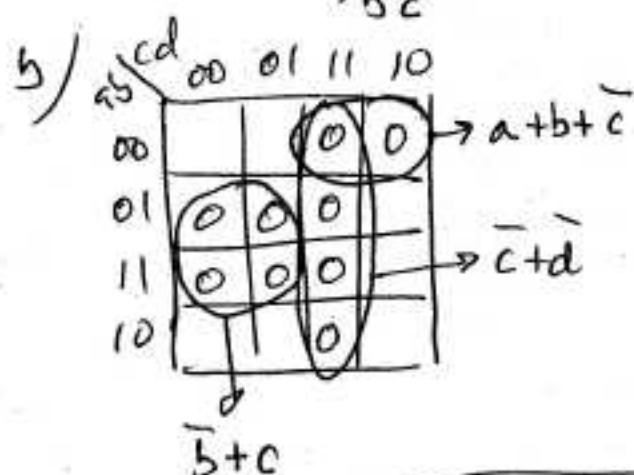
$$f = \sum (0, 1, 6, 8, 9, 10, 14) \\ = \prod (2, 3, 4, 5, 7, 11, 12, 13, 15)$$



$$f = (a+b+\bar{c})(\bar{c}+\bar{d})(\bar{b}+c)$$
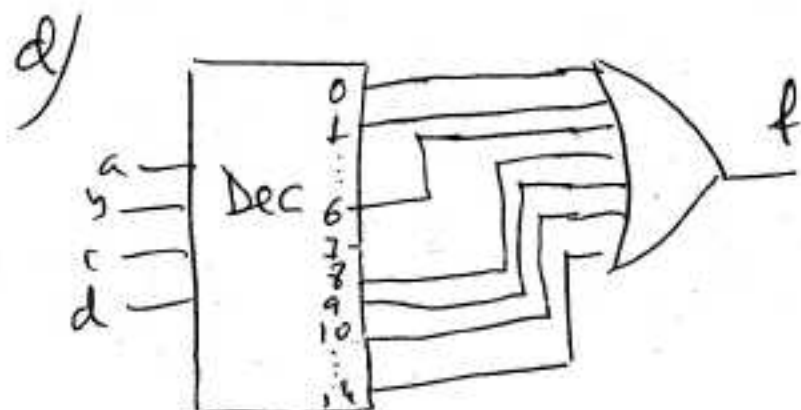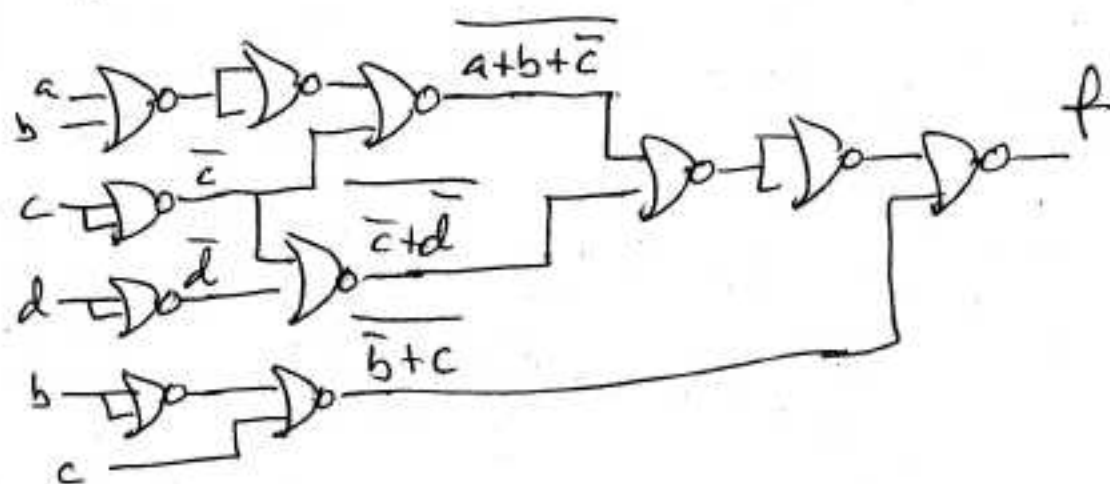
$$c) f = \overline{(a+b+\bar{c})(\bar{c}+\bar{d})(\bar{b}+c)} = \overline{(a+b+\bar{c}) + (\bar{c}+\bar{d}) + \bar{b}+c}$$



e/


a	b	c	d	f
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

c

$c\bar{d}$

$$\overline{cd} = \bar{c} + \bar{d}$$

$c\bar{d}$

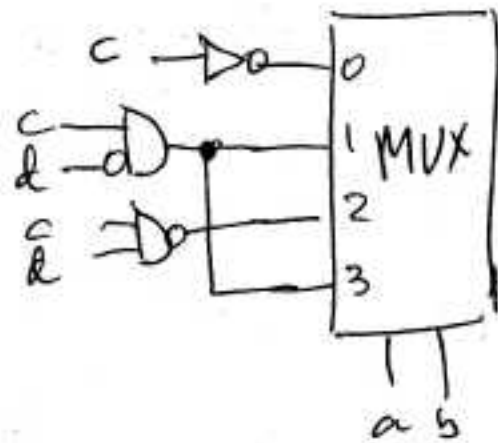

1.2

$$A = E3_{16} = 1110\ 0011$$

$$B = 96_{10} = 0110\ 0000$$

a) $A_{SH} = \begin{cases} 1 & \text{negative} \\ 110\ 0011 & = 99_{10} \end{cases}$

$$A_{SH} = -99_{10}$$

b) $A_{C2} = 1110\ 0011$

$$-A = 0001\ 1101 = 29$$

$$A_{C2} = -29$$

c) $B = 96 = 110\ 0000$

We need an additional bit for the sign: total = 8 bits

$$B_{C2} = 0110\ 0000$$

$$A \quad 1110\ 0011 = -29$$

$$B \quad 0110\ 0000 = +96$$

$$\hline 0100\ 0011 = +67$$

No overflow (operands have different sign)


$$A = 1110\ 0011 = -29$$

$$-B = 1010\ 0000 = -96$$

$$\hline 1000\ 0011 = -125$$

No overflow (operands and result are negative)

1.3

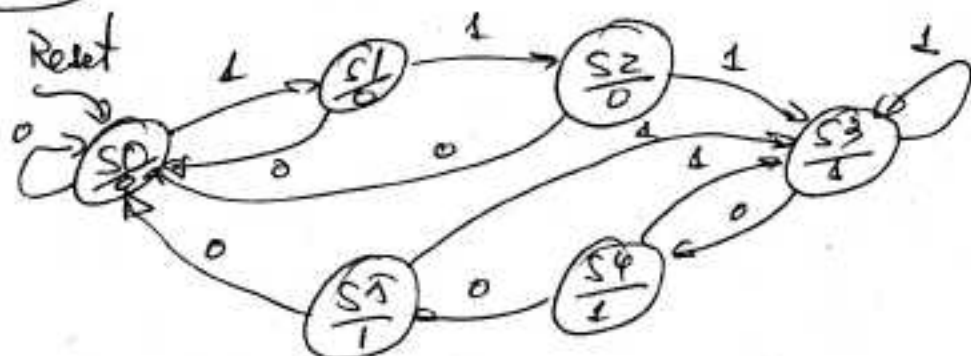

S_0 : Initial f_2, f_1, f_0
 S_1 : $x=1$ 001
 S_2 : 11 010
 S_3 : 111 011
 S_4 : 0 100
 S_5 : 00 101
 S_6 : 000 111

3 TFS

f_2, f_1, f_0	x	D_2	D_1	D_0	z
000	0	0	0	0	
000	1	0	0	1	
001	0	0	0	0	
001	1	0	1	0	
010	0	0	0	0	
010	1	0	1	1	
011	0	1	0	0	
011	1	0	1	1	
100	0	x	x	x	
100	1	x	x	x	
101	0	x	x	x	
101	1	x	x	x	

f_2, f_1, f_0	z
000	0
001	0
010	0
011	1
100	1
101	1
110	x
111	x

f_2, f_1	f_0, x	00	01	11	10
00					
01					1
11		x	x	x	x
10		1			

$$D_2 = f_2 \bar{f}_0 \bar{x} + f_1 f_0 \bar{x}$$

f_2, f_1	f_0, x	00	01	11	10
00				1	
01				1	
11		x	x	x	x
10				1	

$$D_1 = f_1 x + f_2 x + f_0 x = x(f_2 + f_1 + f_0)$$

f_2, f_1	f_0, x	00	01	11	10
00				1	
01				1	
11		x	x	x	x
10		1			

$$D_0 = f_2 \bar{f}_0 + f_2 x + f_1 x + \bar{f}_0 x =$$

f_2, f_1	f_0, x	00	01	11	10
00				1	
01				1	
11		x	x	x	x
10		1			

$$z = f_2 + f_1 f_0$$

e)

