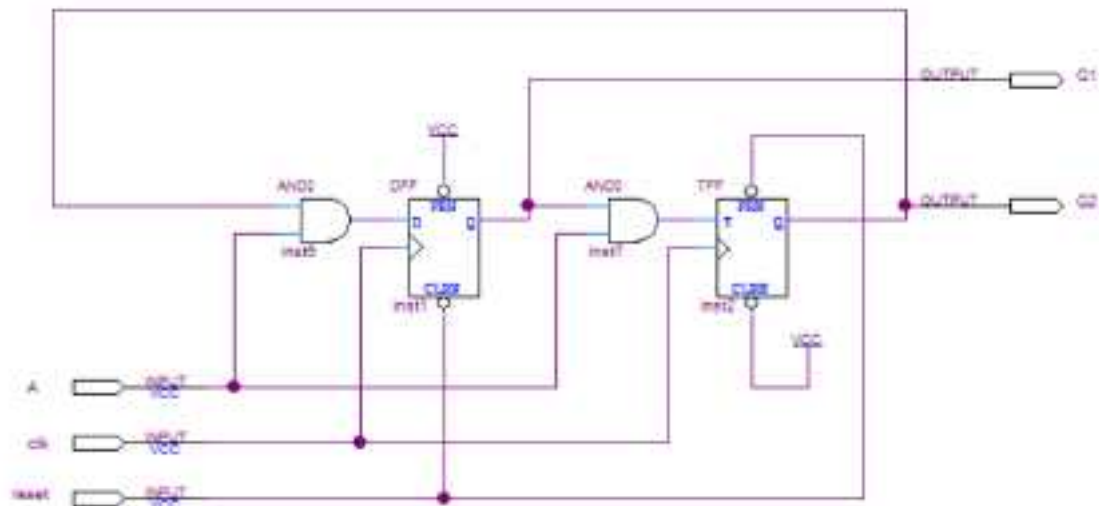


Biestables T

Problem 1 (from Second Term exam, 2015)

Given the following circuit:



- Get the expressions of the state functions D and T.
- Get the transition table of the circuit (use Q1 as MSB and Q2 as LSB).
- Complete the following chronogram (the state value is represented as unsigned integer, with Q1 as the MSB and Q2 as the LSB).

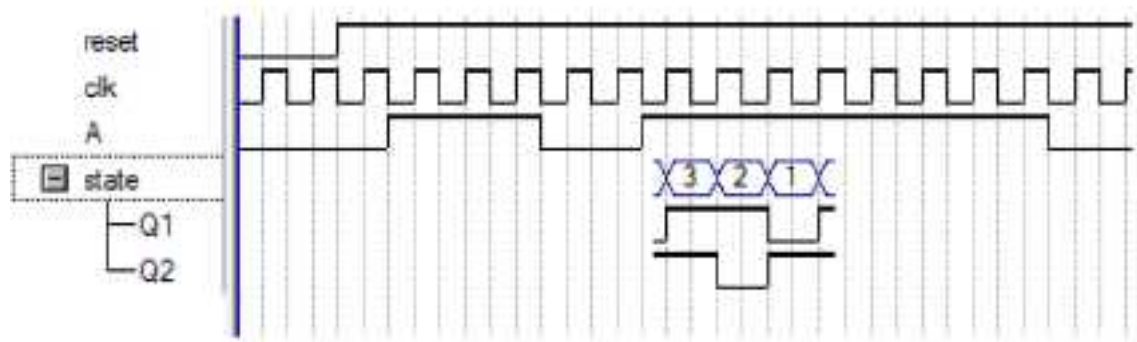


Fig. 1.1

SOLUTION

Question 1: (2,5 points)

a) State functions → $D = A \cdot Q_2$
 $T = A \cdot Q_1$
 (0,25 points)


b) Transition table → looking at the state functions and knowing the flip-flop behaviour (0,25 points)

A	Q ₁	Q ₂	Q ₁ '	Q ₂ '	D	T
0	0	0	0	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	0	0
1	0	1	1	1	1	0
1	1	0	0	1	0	1
1	1	1	1	0	1	1

or


Q ₁	Q ₂	A	Q ₁ '	Q ₂ '	D	T
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	1	0	0
0	1	1	1	1	1	0
1	0	0	0	0	0	0
1	0	1	0	1	0	1
1	1	0	0	1	0	0
1	1	1	1	0	1	1

c)

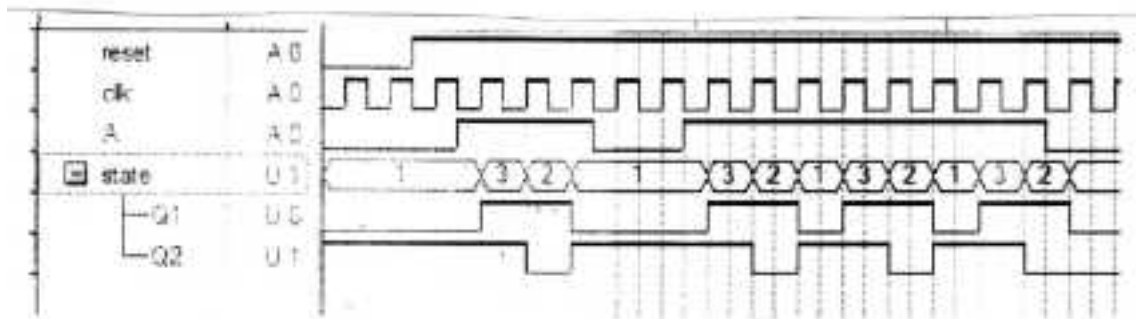

Problem 2:

Complete the following chronogram. Indicate the situations in which the output signals are undefined:

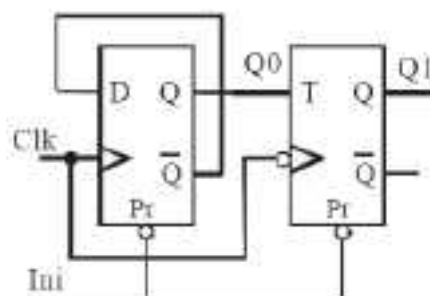


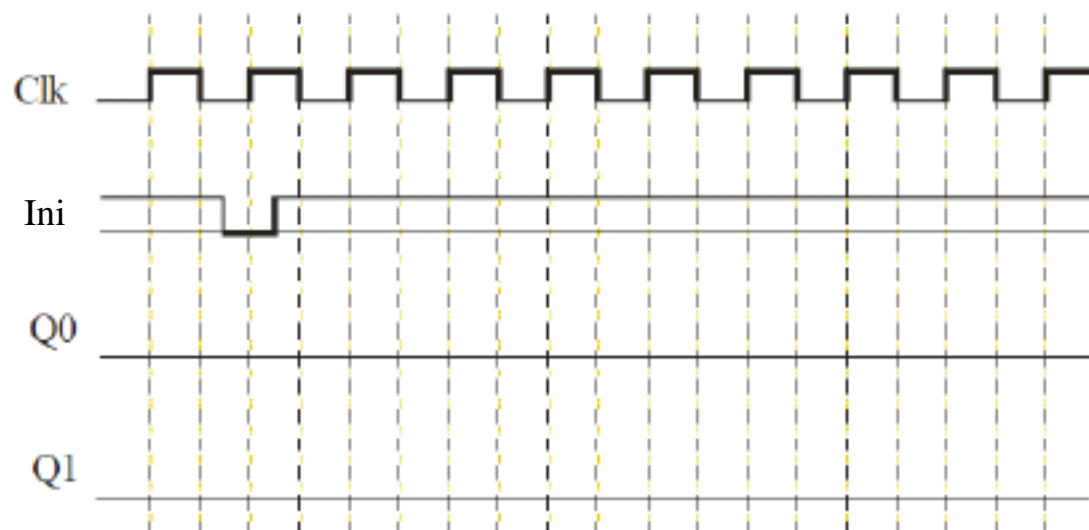




Fig 1.2

SOLUTION

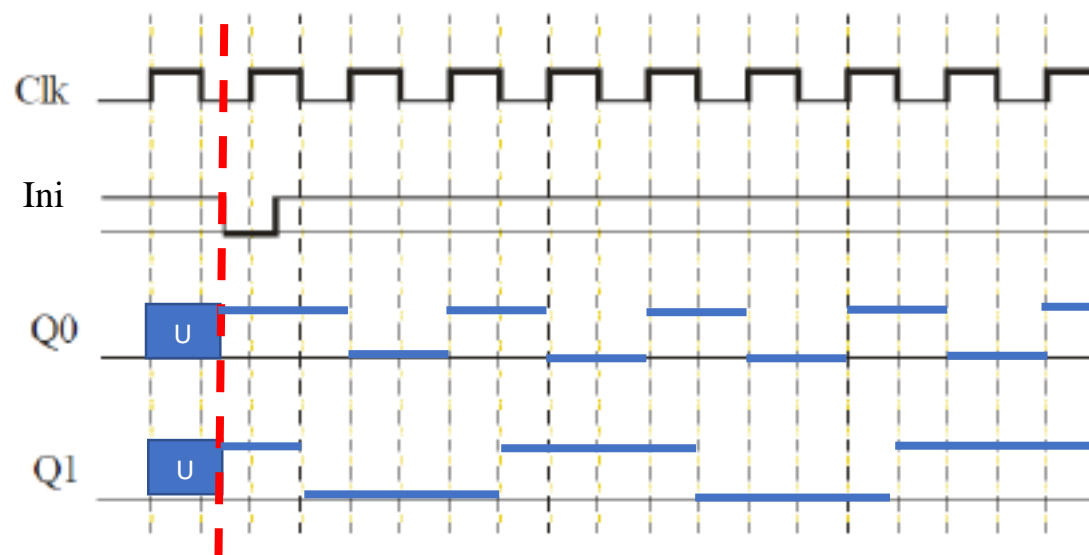

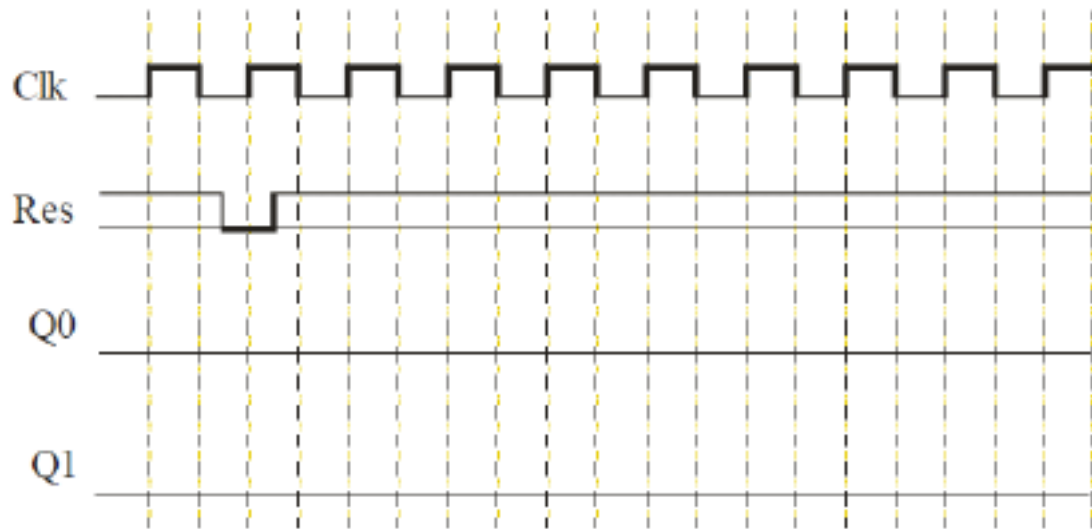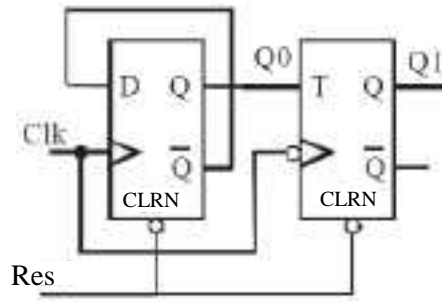Problem 3:

Complete the following chronogram. Indicate the situations in which the output signals are undefined.



SOLUTION

