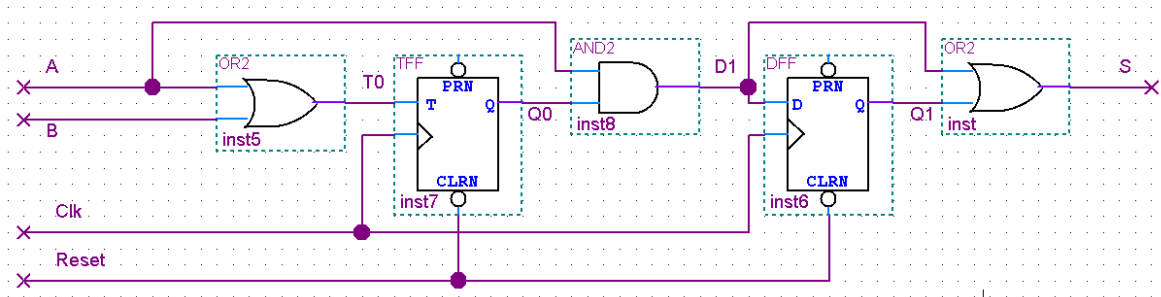




## Question 1


Given the following circuit:



- Write the Boolean expressions of the State functions:
- Write the Boolean expressions of the Output functions:.
- Is it a Moore's Model circuit? Justify why.
- Draw the state transitions graph of the circuit.
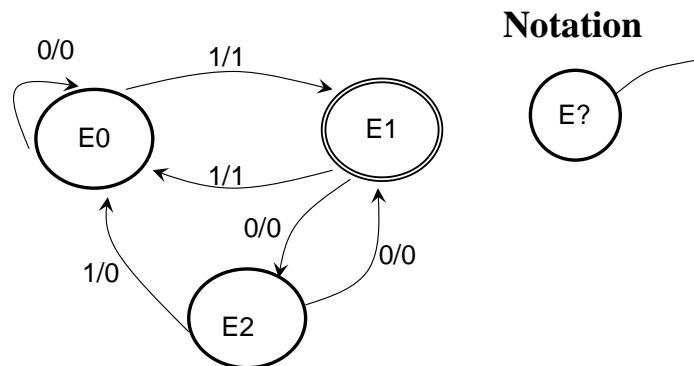
## Question 2

Given the following STG, implement the corresponding synchronous sequential circuit, using T flip-flops.



- Which are the inputs and outputs of the FSM?
- Encode the states. Justify your decision on the number of flip-flops.
- Write the transitions table
- Find simplified expressions for the state and output functions
- Draw the circuit using T flip-flops and a 3:8 decoder (active high outputs), and the necessary additional logic gates (using the minimum possible number of logic gates).



### Question 3

We want to design a sequential circuit which can remotely control the operation of the door of a garage. In order to operate the door of garage, the remote controller sends one of the following cyclic sequences depending on the selection of the switches S0 and S1.

S1	S0	Sequence:
0	0	3-bit binary counter (natural binary code)
0	1	3-bit Gray's code counter
1	0	3-bit Ring counter
1	1	3-bit Johnson's code

Then, draw the state transition graph of a finite state machine using **Moore's** model for the above described remote control operation.