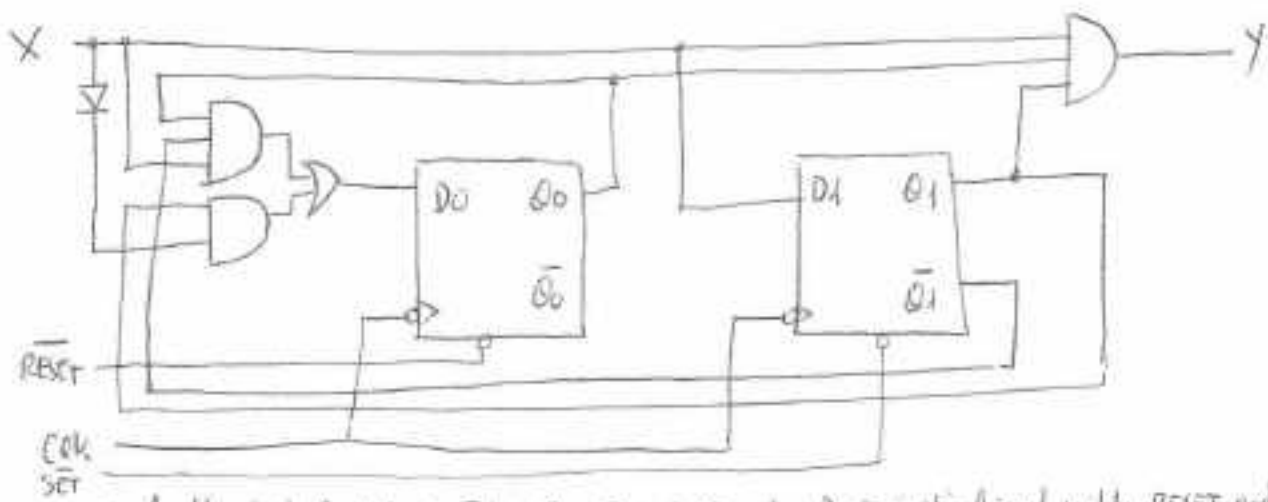


e) The complete circuit is something like this:



→ As the initial state is $E1 \Rightarrow Q_0 = 0$ and $Q_1 = 1$, so it is initialized with RESET and D_0 is initialized with SFT.


* Question 5

4) Inputs: There are 3 inputs for the system, reading the enunciate of the question


- C = vehicle sensor
- T1 = Time for yellow
- T2 = Time for red/green

Outputs: There are 3 outputs for the system, understanding what the question proposes

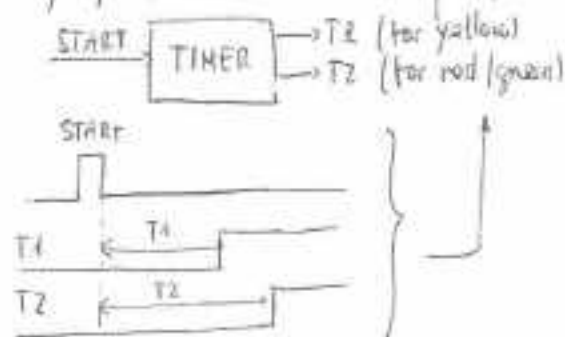- SA = Traffic light for the motorway
- SC = Traffic light for the road
- START = Necessary signal to start the timer for T1 and T2



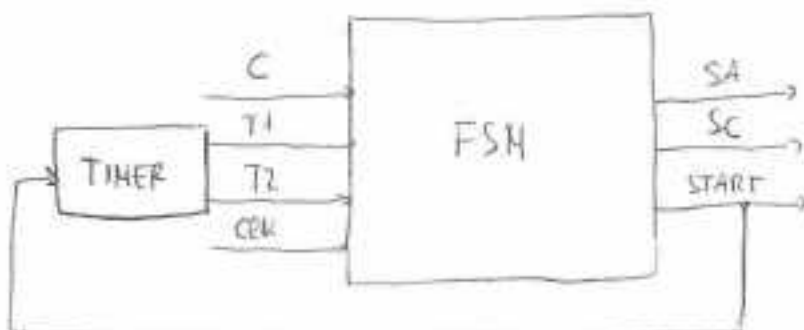Therefore, the block diagram for the circuit is like this:



b) Looking at the notation for the STG, the circuit is Healey