



Surname, Name:

Time: 1h. 40'

Question 1.1 (0.25 points)

Given the decimal integer numbers $A = 88$ and $B = -50$.


- Represent A and B in 2's complement with the minimum possible number of bits.
- Using 2's complement representations for the numbers, perform the operations $A-B$ and $A+B$. Point out if there is overflow in any of this operations and why.

Question 1.2 (0.25 points)

- Draw the 3-bit Gray's Code
- Draw the 3-bit Johnson's Code

Question 1.3 (0.25 points)

Draw the truth table of the following circuit:

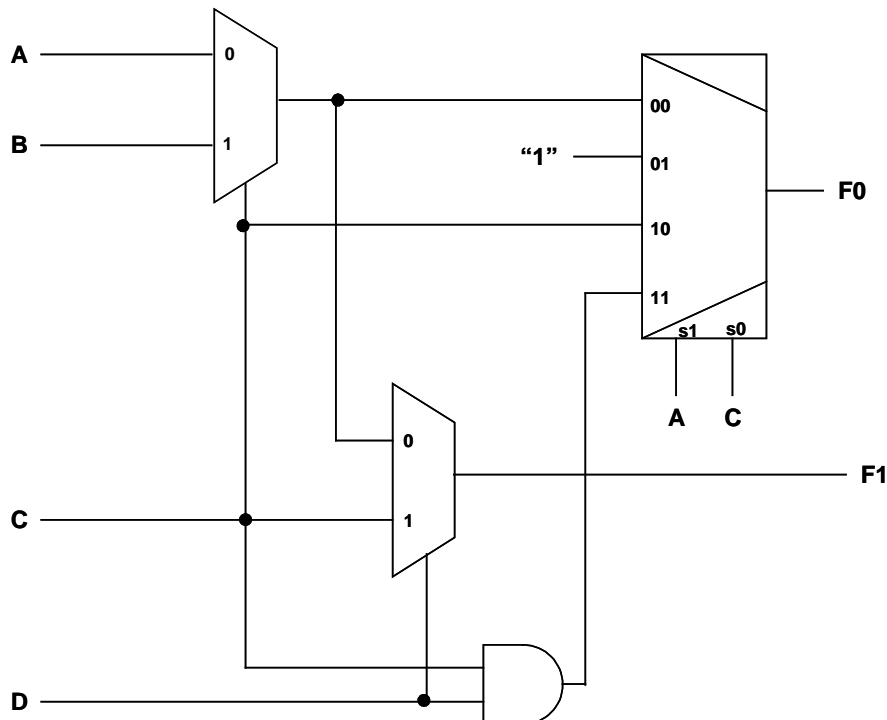



Question 1.4 (0.25 points)


We want to design the following circuit (a 4-bit adder/subtractor).



Where A and B are the data inputs (4-bit), S is the data output (4-bit), Sel is the operation selection ('0' means addition and '1' means subtraction), and OV is an overflow indicator (it is active-high, and it is activated when there is overflow in the operation).

To design this circuit we have available the following components:

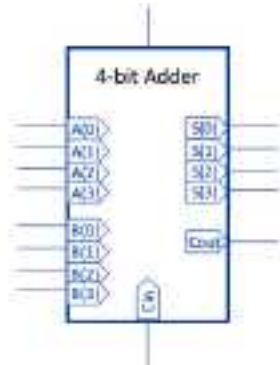- Logic gates
- A 4-bit adder like the one of the figure:



Where A and B are the data inputs (4-bit), S is the data output (4-bit), and Cin/Cout are the carry-in and carry-out of the 4-bit adder.

Design the circuit using these available components.

Problem (1 points)

Given the following logic function:


$$f(a,b,c,d) = \overline{a}cd + \overline{b}(a + c + \overline{d})$$

- Find the most simplified logic expression as a sum of products
- Find the most simplified logic expression as a product of sums
- Implement the logic function with only 2-input NOR gates.
- Implement f with a 4:16 decoder and additional logic gates.
- Implement f with a MUX4 (multiplexer with 4 data inputs) and additional logic gates.



Universidad Carlos III de Madrid
Digital Electronics. 1st midterm exam. March, 2014
Groups 65-69-79-95


* Question 1. a) $A = 88$

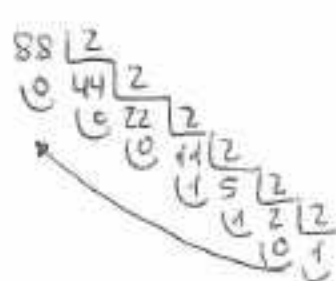

$$\Rightarrow 88_{10} = 1011000_2$$

01011000_{2c}
8 bits

$B = -50$

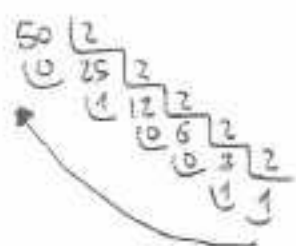

$$\Rightarrow 50_{10} = 110010_2 = 0110010_{2c}$$

\Rightarrow Therefore $-50_{10} = 1001110_{2c}$
7 bits

b) $A - B = 88 - (-50) = 88 + 50$

Adding zero
because this is
a positive number

$$\begin{array}{r} 01011000 (+88) \\ + 00110010 (+50) \\ \hline 10001010 (+138) \end{array}$$

There is overflow, because the sum of 2 positive numbers cannot be equal to a negative number. We can solve this using 9 bits for the operation.


$A + B = 88 - 50$

Adding one
because this is
a positive number

$$\begin{array}{r} 01011000 (+88) \\ + 11001110 (-50) \\ \hline 00100110 (+38) \end{array}$$

There is no overflow, because the result sign is perfectly OK.


* Question 2. a) 3-bit Gray code

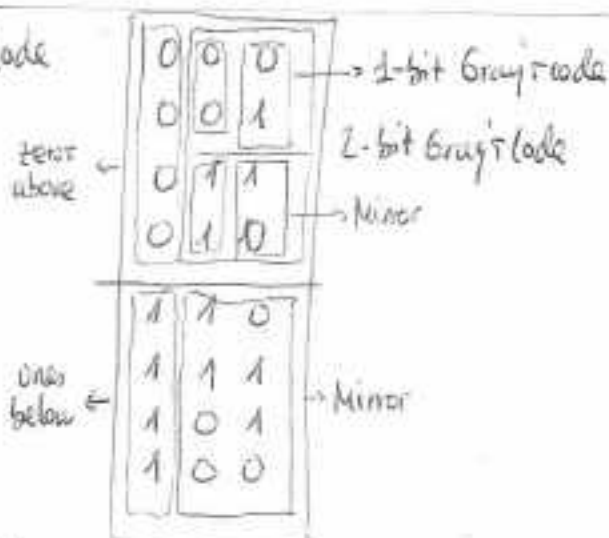

b) 3-bit Johnson's code



* Question 3

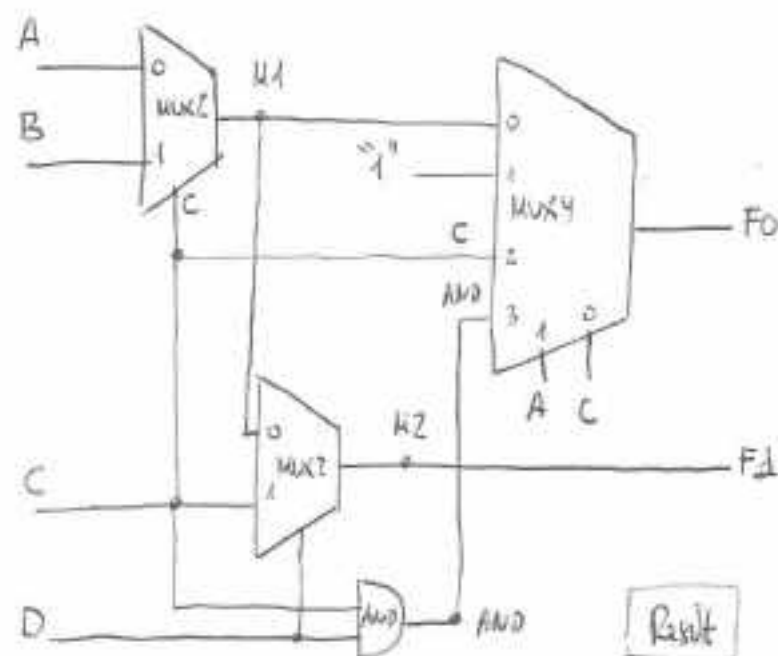

A	B	C	D	M1	M2 = F1	AND	F0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	1
0	0	1	1	0	1	1	1
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	1
1	0	0	0	1	1	0	0
1	0	0	1	1	0	0	0
1	0	1	0	0	0	0	0
1	0	1	1	0	1	1	1
1	1	0	0	1	1	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	1

$F0 = M1$ when $A=0$
 $C=0$
 $F0 = 1$ when $A=0$
 $C=1$
 $F0 = C$ when $A=1$
 $C=0$
 $F0 = AND$ when $A=1$
 $C=1$

$M1 = A$ when $C=0$
 $M1 = B$ when $C=1$

$AND = C \cdot D$


$F1 = M1$ when $D=0$
 $F1 = C$ when $D=1$

* Question 4 : + You have to get the adder/subtractor circuit using the chip given. The trick is to add the necessary gates to this chip in order to get the desired circuit.

- + To subtract in 2-complement, first you have to get the 2-complement of a variable (for example, using the inversion of that variable and adding "1")
- + Now you have to add A and B using the select input to decide if you want to add A and B (addition) or to add A in 2-complement with B (subtraction)
- + You can obtain all of that using the SEL input and every bit of B with 4 XOR gates (connecting the 4 XOR outputs to the 4 B bits in the 4-bit adder) and besides, connecting the SEL input to the C_{in} input of the 4-bit adder, so that:
 - If $SEL=0$, B is not inverted, $C_{in}=0$ and the operation is $A+B$, Set
 - If $SEL=1$, B is inverted, $C_{in}=1$ and the operation is $A-B$
- + To obtain the OV circuit, it is necessary to do the truth table with the most significant bits of the Operands $A(3)$, $B(3)$ and $S(3)$, considering that there is overflow when the sign changes, that means $S(3)=1$ (negative number) when $A(3)=0$ and $B(3)=0$ (positive number), or $S(3)=0$ (positive number) when $A(3)=1$ and $B(3)=1$ (negative number)

$$OV = \overline{A(3)} \cdot \overline{B(3)} \cdot S(3) + A(3) \cdot B(3) \cdot \overline{S(3)}$$

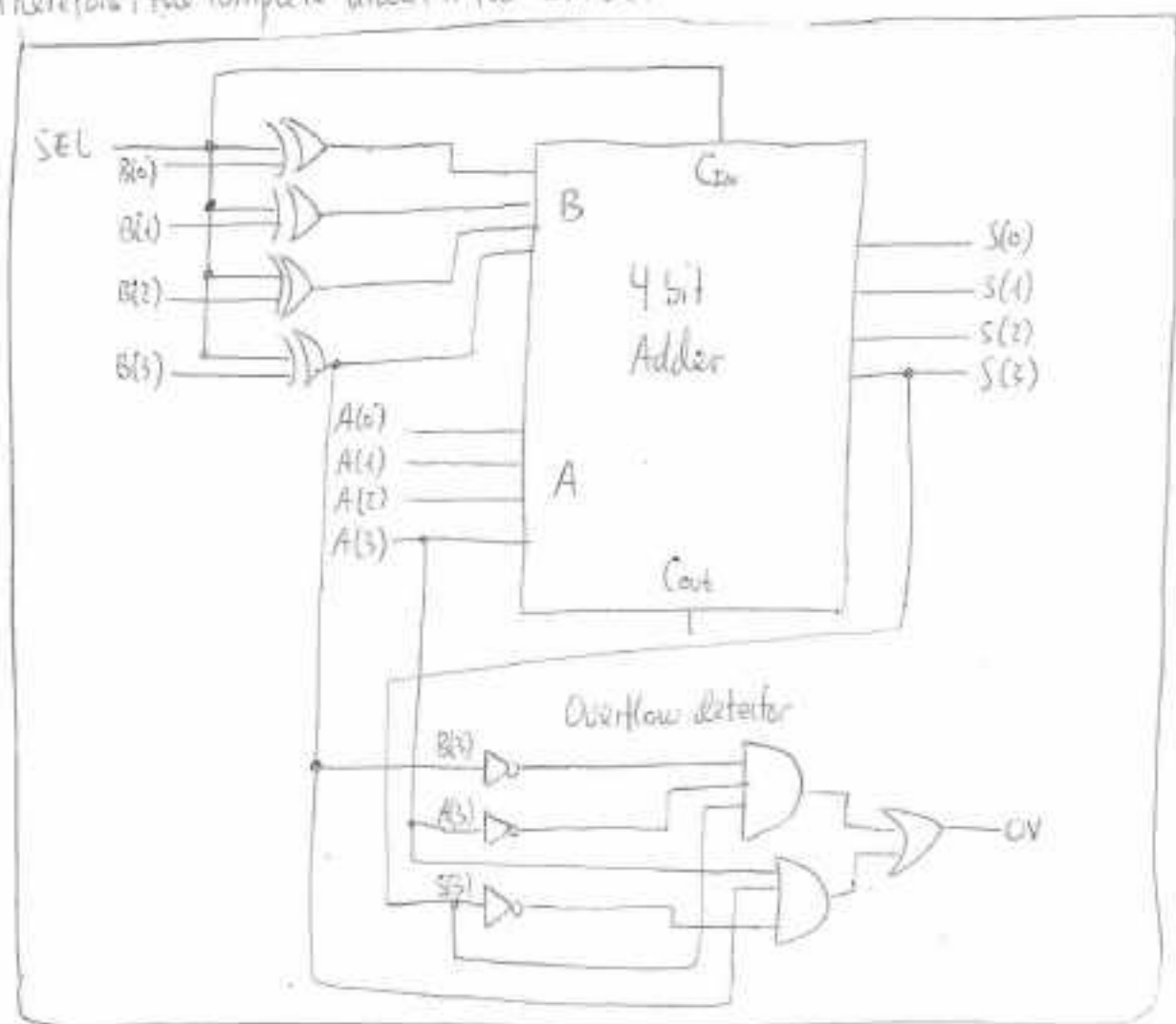+ Therefore, the complete circuit is the next one:



Problem $f = f(a, b, c, d) = \bar{a} \cdot c \cdot d + \bar{b} (a + c + d) = \bar{a} c d + a \bar{b} + \bar{b} c + \bar{b} d$

$$\cdot \bar{a} \cdot c \cdot d = \bar{a} \cdot c \cdot d (b + \bar{b}) = \bar{a} b c d + \bar{a} \bar{b} c d$$

$$\cdot a \bar{b} = a \bar{b} (c + \bar{c}) (d + \bar{d}) = (a \bar{b} c + a \bar{b} \bar{c}) (d + \bar{d}) = a \bar{b} c d + a \bar{b} \bar{c} d + a \bar{b} c \bar{d} + a \bar{b} \bar{c} \bar{d}$$

$$\cdot \bar{b} c = \bar{b} c (a + \bar{a}) (d + \bar{d}) = (a \bar{b} c + \bar{a} \bar{b} c) (d + \bar{d}) = a \bar{b} c d + a \bar{b} \bar{c} d + \bar{a} \bar{b} c d + \bar{a} \bar{b} \bar{c} d$$

$$\cdot \bar{b} d = \bar{b} d (a + \bar{a}) (c + \bar{c}) = (a \bar{b} d + \bar{a} \bar{b} d) (c + \bar{c}) = a \bar{b} c d + a \bar{b} \bar{c} d + \bar{a} \bar{b} c d + \bar{a} \bar{b} \bar{c} d$$

Therefore: $f = \bar{a} b c d + \bar{a} \bar{b} c d + a \bar{b} c d + a \bar{b} \bar{c} d + a \bar{b} c \bar{d} + a \bar{b} \bar{c} \bar{d} + a \bar{b} c d + a \bar{b} \bar{c} d + \bar{a} \bar{b} c d + \bar{a} \bar{b} \bar{c} d + a \bar{b} c d + a \bar{b} \bar{c} d + \bar{a} \bar{b} c d + \bar{a} \bar{b} \bar{c} d$

so

a	b	c	d	f	position
0	0	0	0	1	0
0	0	0	1	0	1
0	0	1	0	1	2
0	0	1	1	1	3
0	1	0	0	0	4
0	1	0	1	0	5
0	1	1	0	0	6
0	1	1	1	1	7
1	0	0	0	1	8
1	0	0	1	1	9
1	0	1	0	1	10
1	0	1	1	1	11
1	1	0	0	0	12
1	1	0	1	0	13
1	1	1	0	0	14
1	1	1	1	0	15

and

ab \ cd	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

a) Sum of products \rightarrow 1st canonical form:

ab \ cd	00	01	11	10
00	1		1	1
01		1		
11				
10	1	1	1	1

$\rightarrow \bar{b} \bar{d}$ (circles at (00,0), (01,1), (10,1))
 $\rightarrow \bar{a} \cdot c \cdot d$ (circles at (01,1), (11,1))
 $\rightarrow a \bar{b}$ (circles at (10,0), (10,1), (11,0), (11,1))

$$f = \bar{b} \bar{d} + \bar{a} \bar{b} + \bar{a} c d$$

b) Product of sums \rightarrow 2nd canonical form:

ab \ cd	00	01	11	10
00	1		1	1
01		1		
11			1	
10	1	1	1	1


$\rightarrow a + c + d$ (circles at (00,0), (01,1), (10,1))
 $\rightarrow \bar{b} + d$ (circles at (01,1), (11,1), (10,1))
 $\rightarrow \bar{a} + \bar{b}$ (circles at (00,0), (01,0), (10,0))

$$f = (\bar{a} + \bar{b}) \cdot (\bar{b} + d) \cdot (a + c + d)$$

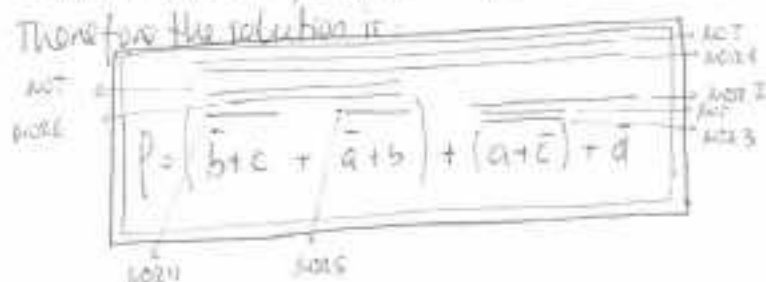
c) We use the first canonical form:

$$f = \overline{b}\overline{c} + a\overline{b} + \overline{a}cd = \overline{b}\overline{c} + a\overline{b} + \overline{a}cd = \overline{b} + \overline{c} + \overline{a} + b + a + \overline{c} + \overline{a}$$

- The not gate is implemented with a NOR gate with the same inputs \Rightarrow
- The NOR with 3 inputs could be implemented as, for example, $(a + \overline{c}) + \overline{a}$ and the AND could be implemented as $\overline{a} + \overline{c}$
- Therefore the solution is:



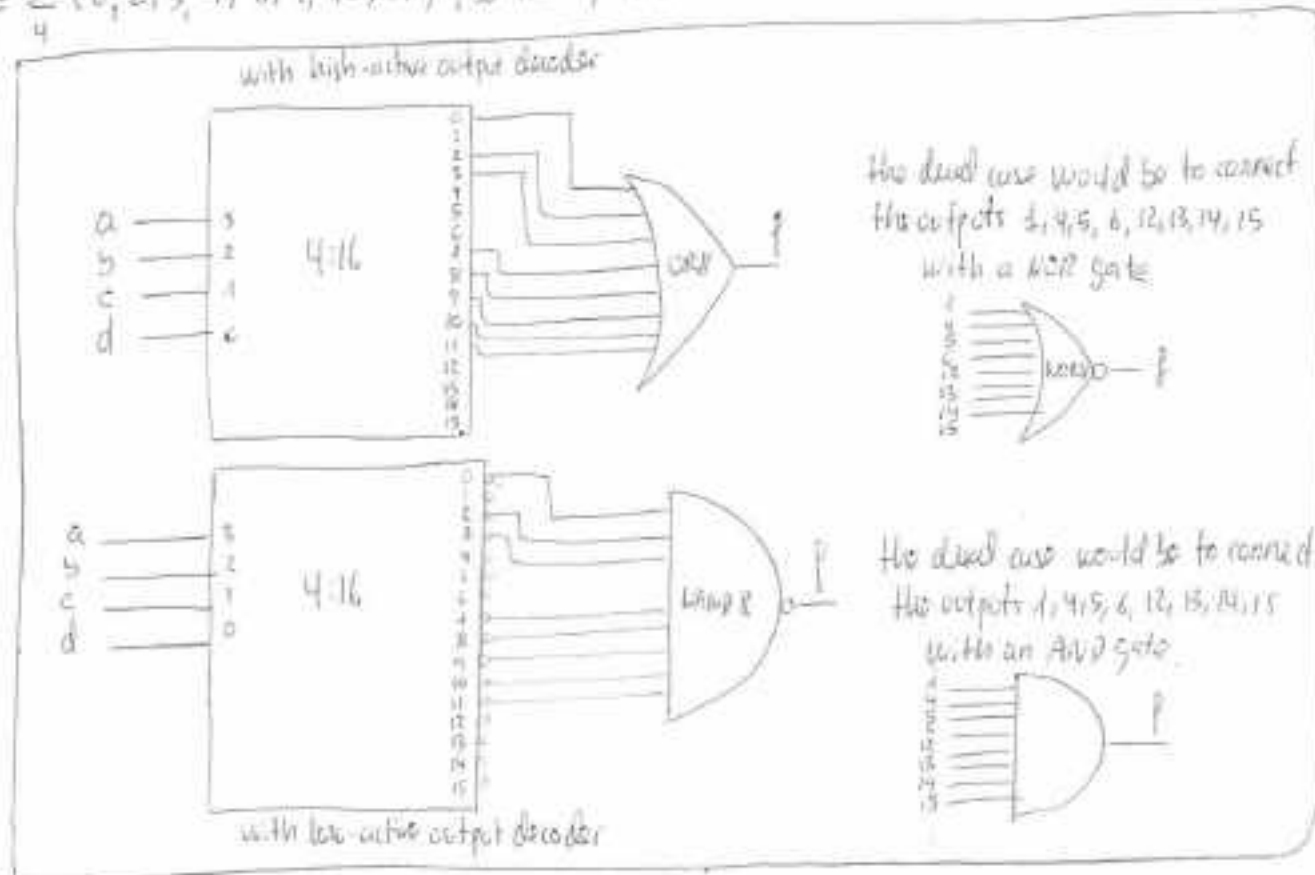d) $f = \sum_4 (0, 2, 3, 7, 8, 9, 10, 11)$, so looking at the truth table there are 4 solutions



e) Looking at the truth table

