

# QUESTION 1

$$\begin{aligned} a) \quad T_0 &= A+B \\ D_1 &= Q_0 A \end{aligned} \quad \left\{ \begin{aligned} Q_0^* &= T_0 \oplus Q_0 \\ Q_1^* &= D_1 \end{aligned} \right.$$


$$b) \quad S = Q_0 A + Q_1$$

c) Nexty's, as  $S$  is a function that depends on the input  

$$S = f(A, Q_0, Q_1)$$

d)

A	B	$Q_0$	$Q_1$	$Q_0^*$	$Q_1^*$	S
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	1	0	0
0	0	1	1	1	0	1
0	1	0	0	1	0	0
0	1	0	1	1	0	1
0	1	1	0	0	0	0
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	1
1	0	1	0	0	1	0
1	0	1	1	0	1	1
1	1	0	0	1	0	0
1	1	0	1	1	0	1
1	1	1	0	0	1	0
1	1	1	1	0	1	1

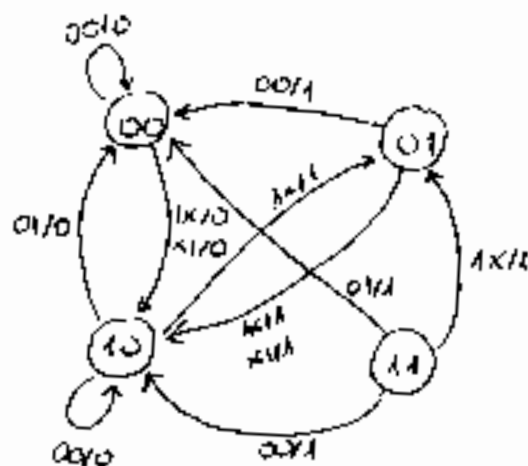

# QUESTION 2

4) A input  
1 B output

b)

state	$Q_1, Q_0$
$E_0$	0 0
next $\rightarrow E_1$	0 1
$E_2$	1 0

2 Flip-Flops to encode 3 states ( $2^2 > 3$ )

c)

$Q_1, Q_0, A$	$Q_1^+, Q_0^+$	$B$	$T_1$	$T_0$
0 0 0	0 0	0	0	0
0 0 1	0 1	1	0	1
0 1 0	1 0	0	1	1
0 1 1	0 0	1	0	1
1 0 0	0 1	0	1	1
1 0 1	0 0	0	1	0
1 1 0	x x	x	x	x
1 1 1	x x	x	x	x

d)

$Q_1/Q_0, A$	00	01	11	10
0	0	1	1	0
1	0	0	x	x

$$B = Q_1 A$$

$Q_1/Q_0, A$	00	01	11	10
0	0	0	0	1
1	1	1	x	x

$$T_1 = Q_1 + Q_0 \bar{A}$$

$Q_1/Q_0, A$	00	01	11	10
0	0	1	1	1
1	1	0	x	x

$$T_0 = Q_0 + Q_1 \bar{A} + Q_0 A = Q_0 + (Q_1 \oplus A)$$

$$T_0 = (Q_1 + Q_0 + A)(\bar{Q}_1 + \bar{A})$$

Note with D Flip-Flops (considered as correct in the corrections)



$Q_1/Q_0, A$	00	01	11	10
0	0	0	0	1
1	0	0	x	x

$$D_1 = Q_1^+ = Q_0 \bar{A}$$

$Q_1/Q_0, A$	00	01	11	10
0	0	1	0	0
1	1	0	x	x

$$D_0 = Q_0^+ = \bar{Q}_1 \bar{Q}_0 A + Q_1 \bar{A}$$

d)  
2

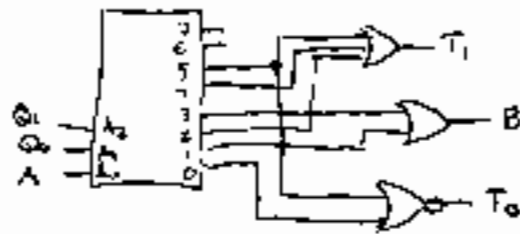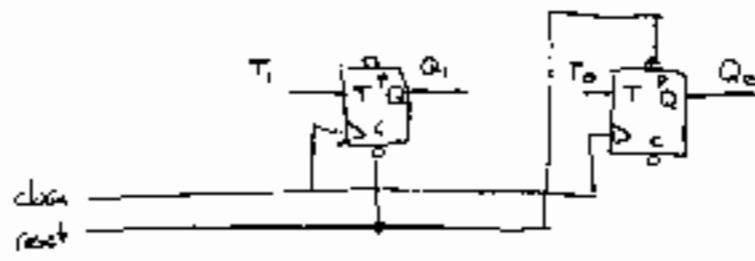




### Question 3

We want to design a sequential circuit which can remotely control the operation of the door of a garage. In order to operate the door of garage, the remote controller sends one of the following cyclic sequences depending on the selection of the switches S0 and S1.

S1	S0	Sequence:
0	0	3-bit binary counter (natural binary code)
0	1	3-bit Gray's code counter
1	0	3-bit Ring counter
1	1	3-bit Johnson's code

Then, draw the state transition graph of a finite state machine using Moore's model for the above described remote control operation.
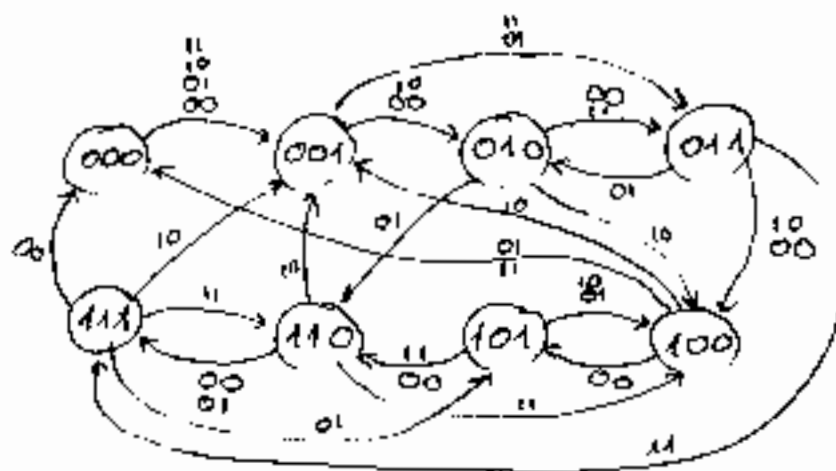
$$\text{output} = \text{state} = Q_2 Q_1 Q_0$$



Gray's code:

0 0 0  
0 0 1  
0 1 1  
0 1 0  
1 1 0  
1 1 1  
1 0 1  
1 0 0

Ring counter:

0 0 1  
0 1 0  
1 0 0

Johnson's code

0 0 0  
0 0 1  
0 1 1  
1 1 1  
1 1 0  
1 0 0